
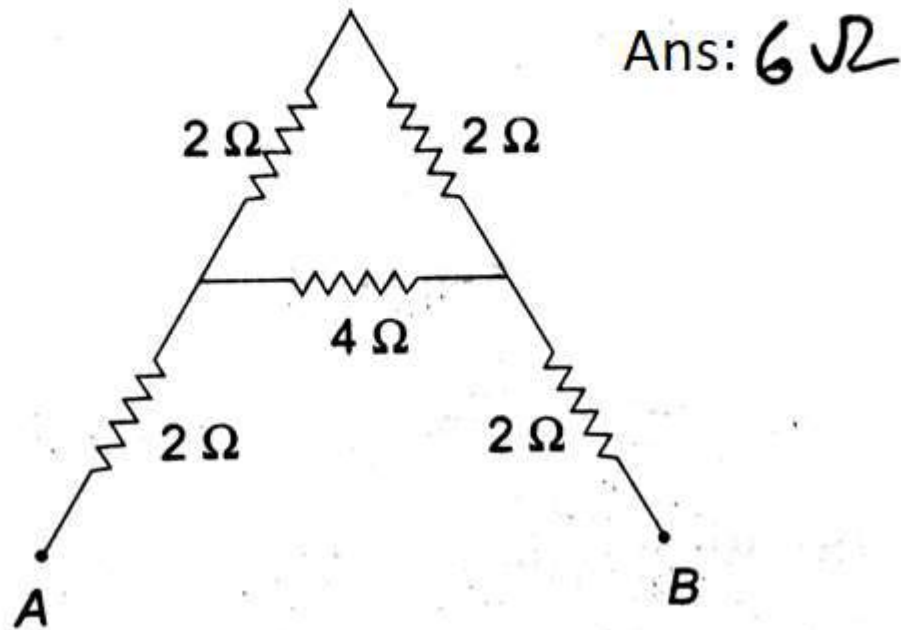


Class 10 Chapter Electricity Circuit Problems

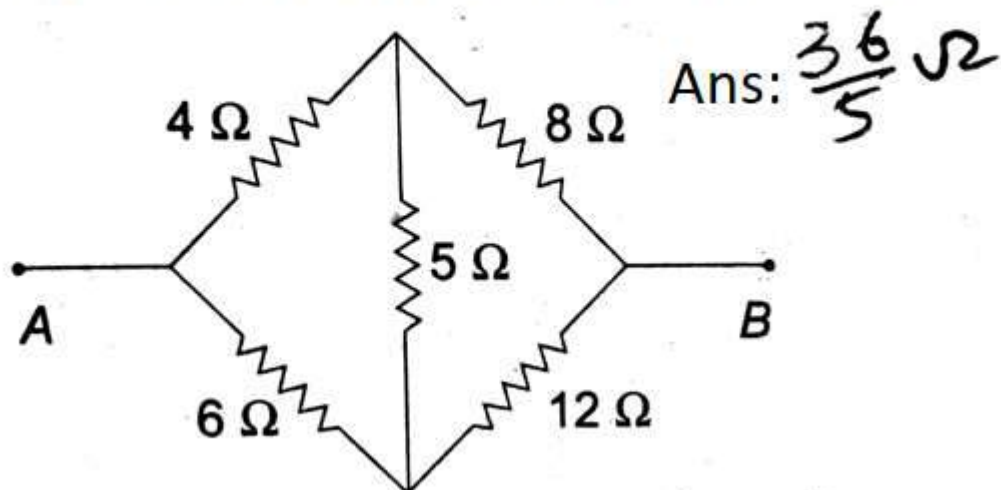
Q. What is the resistance between A and B



Q. What is the resistance between A and B




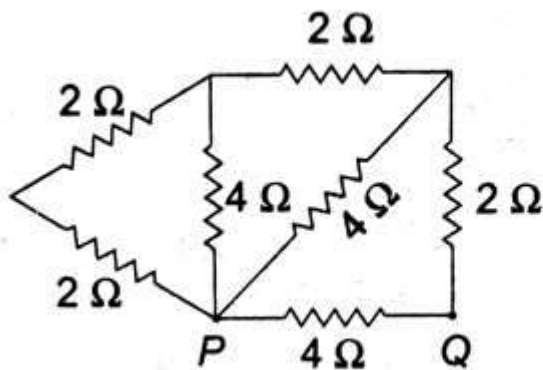Q. What is the resistance between P and Q




Ans: $2\ \Omega$

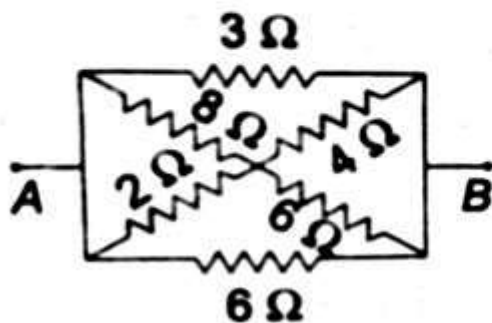Q. What is the resistance between A and B




Ans: $\frac{4}{3}\ \Omega$

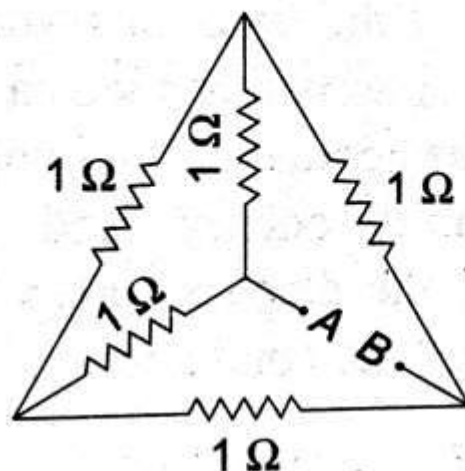Q. What is the resistance between A and B




Ans: $1\ \Omega$

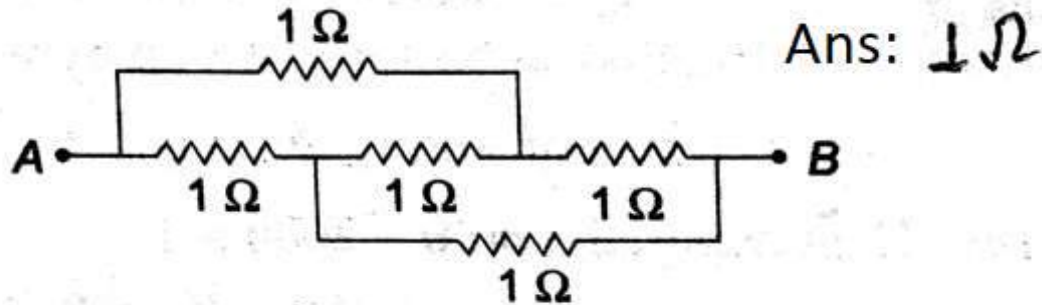Q. What is the resistance between A and B




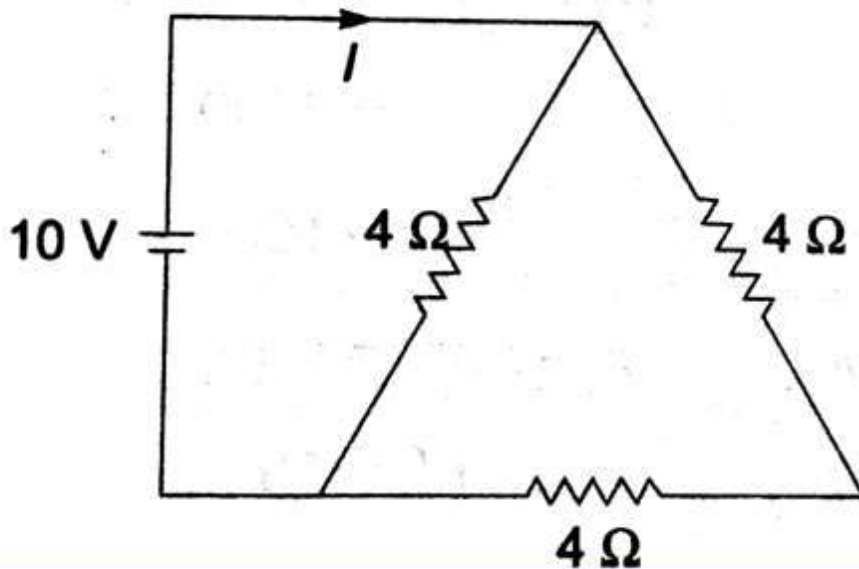Q. What is the current in given network ?



Ans: $R = \frac{8}{3}\Omega$ $I = \frac{15}{4}A$

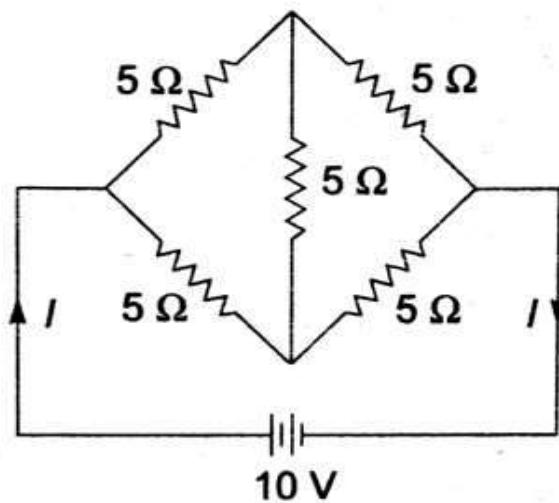
Q. What is the current in given network ?



$$R = 5 \text{ ohm}$$

$$I = 2 \text{ A}$$

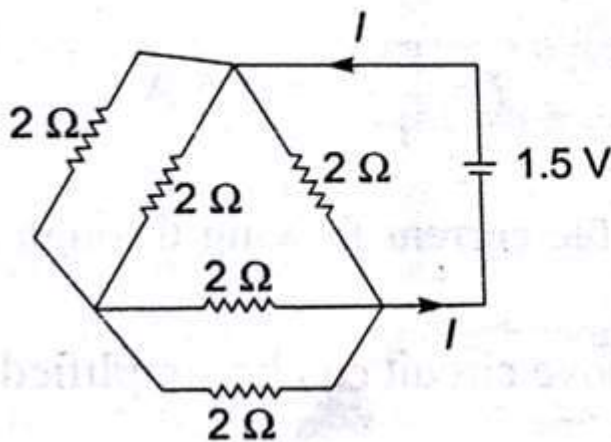Q. what is the electric current in the given circuit



$$R = 1.5 \Omega$$

$$I = \frac{1.5}{1} = 1.5 \text{ A}$$

Q. What is the resistance between A and B in following circuit?

Ans: 1Ω

