

10th Solved Numerical: Ch: Electricity

EXAMPLE How much work is done in moving a charge of 3 C across two points having a potential difference 15 V?

SOLUTION

Here,

$$\text{Potential difference } (V) = 15 \text{ V}$$

$$\text{Charge } (Q) = 3 \text{ C}$$

$$\text{Work done } (W) = ? \quad (\text{to be calculated})$$

$$\text{We know,} \quad V = \frac{W}{Q}$$

Putting the values in the above equation, we get

$$15 \text{ V} = \frac{W}{3 \text{ C}}$$

$$W = 15 \text{ V} \times 3 \text{ C}$$

$$W = 45 \text{ J}$$

Thus, work done in moving the charge is 45 J.

EXAMPLE How much energy is given to each coulomb of charge passing through a 6 V battery?

SOLUTION

Here,

$$\text{Potential difference } (V) = 6 \text{ V}$$

$$\text{Charge } (Q) = 1 \text{ C}$$

$$\text{Work done } (W) = ? \quad (\text{to be calculated})$$

$$\text{We know,} \quad V = \frac{W}{Q}$$

Putting the values in the above equation, we get

$$6 \text{ V} = \frac{W}{1 \text{ C}}$$

$$W = 6 \text{ V} \times 1 \text{ C}$$

$$W = 6 \text{ J}$$

Thus, work done in moving the charge is 6 J.

EXAMPLE If 3×10^{-3} J of work is done in moving a particle carrying a charge of 15×10^{-6} C from infinity to a point P, what will be the potential at the point P?

SOLUTION

Here,

$$\text{Work done } (W) = 3 \times 10^{-3} \text{ J}$$

$$\text{Charge } (Q) = 15 \times 10^{-6} \text{ C}$$

$$\text{Electric potential } (V) = ? \quad (\text{to be calculated})$$

$$\text{We know,} \quad V = \frac{W}{Q}$$

$$V = \frac{3 \times 10^{-3} \text{ J}}{15 \times 10^{-6} \text{ C}}$$

$$V = \frac{3 \times 10^3}{15} \text{ V}$$

$$V = 200 \text{ V}$$

Thus, the potential at the point P is 200 V

EXAMPLE 80 J of work is done in moving a charge of 4 C from one terminal of the battery to another. What is the potential difference of the battery?

SOLUTION

Here,

$$\text{Work done } (W) = 80 \text{ J}$$

$$\text{Charge } (Q) = 4 \text{ C}$$

$$\text{Potential difference } (V) = ? \quad (\text{to be calculated})$$

$$\text{We know,} \quad V = \frac{W}{Q}$$

Putting the values in the above equation, we get

$$V = \frac{80 \text{ J}}{4 \text{ C}}$$

$$V = 20 \text{ V}$$

Thus, the potential difference of the battery is 20 V

EXAMPLE A current of 0.2 A is drawn by the filament of an electric bulb for 30 minutes. Find the amount of electric charge that flows through the circuit.

SOLUTION Here,

$$\text{Electric current } (I) = 0.2 \text{ A}$$

$$\text{Time } (t) = 30 \text{ minutes} = 1800 \text{ s}$$

Amount of electric charge

$$(Q) = ? \quad (\text{to be calculated})$$

$$\text{We know,} \quad I = \frac{Q}{t}$$

Putting the values in the above equation, we get

$$0.2 \text{ A} = \frac{Q}{1800 \text{ s}}$$

$$Q = 0.2 \text{ A} \times 1800 \text{ s}$$

$$Q = 360 \text{ C}$$

Thus, the amount of electric charge that flows through the circuit is 360 C.

Visit Regularly

www.jsuniltutorial.weebly.com/

EXAMPLE 5 C of charge flows through any cross-section of a conductor in 10 seconds. What is the current flowing through the conductor?

SOLUTION Here,

$$\text{Charge flowing } (Q) = 5 \text{ C}$$

$$\text{Time taken } (t) = 10 \text{ s}$$

$$\text{Current flowing } (I) = ? \quad (\text{to be calculated})$$

$$\text{We know, } I = \frac{Q}{t}$$

Putting the values in the above equation, we get

$$I = \frac{5 \text{ C}}{10 \text{ s}} = 0.5 \text{ A}$$

Thus, the current flowing through the conductor is 0.5 A.

EXAMPLE A battery of three cells of 2 V each, a 5 Ω resistor, an 8 Ω resistor, a 12 Ω resistor and a plug key are all connected in series. (a) Draw a circuit diagram (b) Find the resultant resistance.

SOLUTION

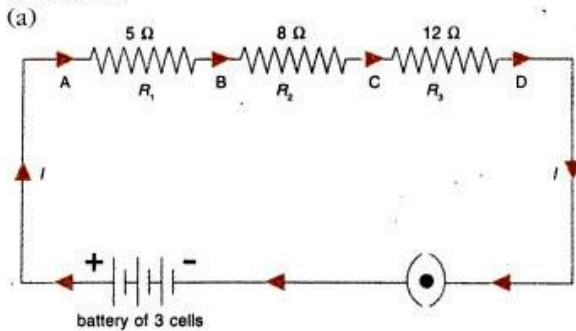


Fig. 4.27

(b) Here, $R_1 = 5 \Omega$, $R_2 = 8 \Omega$, $R_3 = 12 \Omega$

We know,

Total resistance (in series)

$$R = R_1 + R_2 + R_3$$

$$\therefore R = 5 \Omega + 8 \Omega + 12 \Omega$$

$$R = 25 \Omega$$

Thus, the resultant resistance is equal to 25 Ω.

EXAMPLE What will be the resistance of a metal wire of length 2 m and area of cross-section $1.25 \times 10^{-6} \text{ m}^2$, if the resistivity of the metal is $1.6 \times 10^{-8} \Omega \text{ m}$?

SOLUTION

We know

$$\rho = \frac{R \times A}{l}$$

Here, Resistance (R) = ? (to be calculated)

Area of cross-section (A) = $1.25 \times 10^{-6} \text{ m}^2$

Length (l) = 2 m

Resistivity of the metal (ρ) = $1.6 \times 10^{-8} \Omega \text{ m}$

So, putting these values in the above formula, we get

$$1.6 \times 10^{-8} \Omega \text{ m} = \frac{R \times 1.25 \times 10^{-6} \text{ m}^2}{2 \text{ m}}$$

$$\text{or } R = \frac{2 \text{ m} \times 1.6 \times 10^{-8} \Omega \text{ m}}{1.25 \times 10^{-6} \text{ m}^2}$$

$$\text{or } R = \frac{2 \times 1.6 \times 10^{-8+6} \Omega}{1.25}$$

$$\text{or } R = \frac{2 \times 1.6 \times 10^{-2} \Omega}{1.25}$$

$$\text{or } R = 2.56 \times 10^{-2} \Omega$$

Thus, the resistance of the metal wire is $2.56 \times 10^{-2} \Omega$

Example An electric bulb draws a current of 0.2 A when the voltage is 220 volts. Calculate the amount of electric charge flowing through it in one hour. [Delhi 2004 C]

Ans. $I = 0.2 \text{ A}$, $V = 220 \text{ volt}$ $t = 1 \text{ h} = 3600 \text{ s}$

$$\text{We know, } I = \frac{q}{t} \quad q = I \times t = 0.2 \times 3600 = 720 \text{ coulomb}$$

Example A bulb is rated at 5.0 volt, 100 mA. Calculate its (i) power and (ii) resistance.

Ans. (i) $V = 5.0 \text{ volt}$,

$I = 100 \text{ mA}$

$$\text{Power} = VI = 5 \times 100 \times 10^{-3} = 0.5 \text{ watt}$$

(ii) Resistance = $R = \frac{V}{I}$

$$= \frac{5}{100 \times 10^{-3}} = \frac{5000}{100} = 50 \Omega$$

Visit Regularly

www.jsuniltutorial.weebly.com/

Example Calculate the amount of charge that would flow in 30 minutes through the element of an electric bulb drawing a current of 0.4 A.

Ans. $t = 30 \text{ min} = 30 \times 60 = 1800 \text{ s}$
 $I = 0.4 \text{ A}$
 $q = It = 0.4 \times 1800 = 720 \text{ coulomb}$

Example Two resistors with resistances 10 ohm and 15 ohm are to be connected to a battery of emf 5 V so as to obtain

- (i) maximum current
- (ii) minimum current
- (a) How will you connect the resistances in each case ?
- (b) Calculate the strength of total current in the circuit in the two cases.

Ans. (a) (i) Resistance has to be small, so parallel connection.

(ii) Series connection will have maximum resistance, so minimum current.

(b) $I_{\min} = \frac{5}{10+15} = \frac{1}{5} \text{ A}$

$I_{\max} = \frac{5}{\frac{150}{25}} = \frac{5}{6} \text{ A}$

Example An electric iron has a rating of 750 W, 220 V. Calculate (i) current passing through it, and (ii) its resistance, when in use.

Ans. (i) $\text{Current} = \frac{\text{Power}}{\text{Voltage}} = \frac{750}{220} = 3.41 \text{ A}$

(ii) $\text{Resistance} = \frac{\text{Voltage}}{\text{Current}} = \frac{220}{3.41} = 64.5 \Omega$


Example An electric iron has a rating of 1000 W, 220 V. When in use calculate for it

- (i) current passing through it,
- (ii) its resistance [Delhi 2007]

Ans. (i) $\text{Power} = \text{Current} \times \text{Voltage}$
 $\therefore \text{Current} = \frac{\text{Power}}{\text{Voltage}} = \frac{1000}{220} \text{ A}$
 $= 4.545 \text{ A}$

(ii) $\text{Resistance} = \frac{\text{Voltage}}{\text{Current}} = \frac{220}{4.545} \Omega$
 $= 48.4 \Omega$

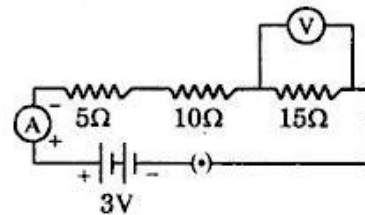Example What are the likely readings of the ammeter and the voltmeter in the circuit shown here ?



Ans. The ammeter reading would be

$$\frac{3}{5+10+15} \text{ A} = \frac{3}{30} \text{ A} = 0.1 \text{ A}$$

The voltmeter reading would be

$$0.1 \times 15 \text{ V} = 1.5 \text{ V}$$

Example A 220 V line supplies a total current of 5 A to N resistors (each of value 176 Ω) connected in parallel. What is the value of N ?

Ans. The total resistance of the parallel combination of N resistors


$$= \frac{220}{5 \text{ A}} \text{ V} = 44 \text{ ohm}$$

$$\therefore \frac{1}{44} = \frac{1}{176} + \frac{1}{176} + \dots \text{ N times}$$

$$= \frac{N}{176}$$

$$\therefore N = \frac{176}{44} = 4$$

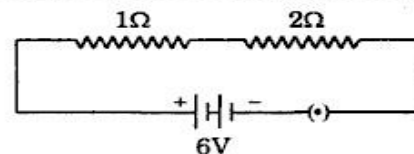Example Calculate the power used in the 2 Ω resistor in the circuit shown here.




Ans. Current through the circuit

$$= \frac{6 \text{ V}}{(1+2) \Omega} = 2 \text{ A}$$

\therefore Power used in the 2Ω resistor

$$= I^2 R = (2)^2 \times 2 \text{ watt} = 8 \text{ W}$$

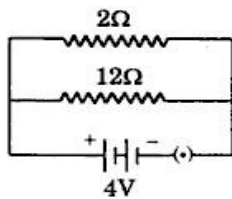Example Calculate the power used in the $2\ \Omega$ resistor in the circuit shown here.



Ans. Current through the $2\ \Omega$ resistor

$$= \frac{4V}{2\ \Omega} = 2\ \text{A}$$

$$\therefore \text{Power used in the } 2\ \Omega \text{ resistor}$$

$$= I^2 R$$

$$= (2)^2 \times 2\ \text{watt} = 8\ \text{W}$$

Example When N identical electric bulbs, each rated as $11\ \text{W}$, $220\ \text{V}$ are connected in parallel across a $220\ \text{V}$ supply line, the total current drawn is $5\ \text{A}$. What is the value of N ?

Ans. Resistance of each bulb

$$= \frac{220 \times 220}{11}\ \text{ohm}$$

$$= 4400\ \text{ohm}$$

$$\therefore \text{Resistance of the parallel combination of } N \text{ such bulbs} = \frac{4400}{N}\ \text{ohm}$$

$$\therefore \frac{4400}{N} = \frac{220}{5}$$
 or
$$N = \frac{4400 \times 5}{220} = 100$$

$$\therefore 100 \text{ bulbs are needed in this case.}$$

Example An electric heater of resistance $8\ \Omega$ draws $15\ \text{A}$ from the service mains 2 hours. Calculate the rate at which heat is developed in the heater.

Ans. Rate of development of heat $= I^2 R$

$$= (15)^2 \times 8\ \Omega = 1800\ \Omega$$

Example A wire of resistance $20\ \text{ohm}$ is bent in the form of a closed circle. What is the effective resistance between the two points at the ends of any diameter of the circle?

Ans. Let R be the required effective resistance.

Then

$$\frac{1}{R} = \frac{1}{10} + \frac{1}{10} = \frac{2}{10} = \frac{1}{5}$$

$$R = 5\ \Omega$$

Example A wire of resistance $10\ \text{ohm}$ is bent in the form of a closed circle. What is the effective resistance between the two points at the ends of any diameter of the circle?

Ans. Let R be the effective resistance.

Then

$$\frac{1}{R} = \frac{1}{5} + \frac{1}{5} = \frac{2}{5}$$

$$\therefore R = \frac{5}{2}\ \Omega = 2.5\ \Omega$$

Visit Regularly

www.jsuniltutorial.weebly.com/