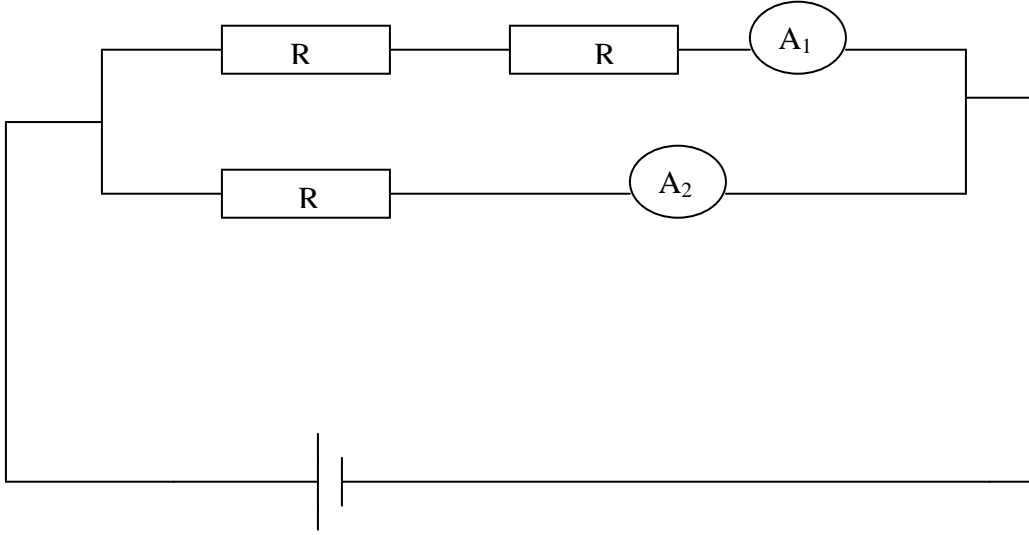


## Chapter - 12

### Electricity

(1 Mark Questions)

**Q-1** In the given figure what is the ratio of current in  $A_1$ , and  $A_2$



---

Ans- $V=IR$        $V=\text{const.}$   
 $I \propto 1/R$        $I_1/I_2 = R/2R$        $I_1/I_2 = 1/2$

**Q-2** A wire of resistance  $R$  is bent in form of a closed circle, what is the resistance across a diameter of the circle?

Ans- $1/R' = 1/(R/2) + 1/(R/2)$        $R' = R/4.$

**Q-3** A charge of  $6\text{ C}$  is moved between two points  $P$  and  $Q$  having , potential  $10\text{V}$  and  $5\text{V}$  respectively. Find the amount of work done.

Ans- $W=q(V_2-V_1)=6(10-5)=30$  joule

**Q-4** Name the physical quantity whose SI unit is  $\text{JC}^{-1}$ .

Ans-Potential

### (2 Marks Questions)

**Q-1** Two wires of equal cross sectional area , one of copper and other of manganin have same resistance. Which one will be longer?

Ans- $R=\rho L/A$  ( $R,A=\text{const. } L=1/\rho$ )

$\rho_{\text{manganin}} > \rho_{\text{copper}}$

$L_{\text{copper}} > L_{\text{manganin}}$

**Q-2** A Rectangular block of iron has dimensions  $L \times L \times b$ . What is the resistance of the block measured between the two square ends ? Given  $\rho =$  resistivity.

Ans- $R=\rho b/L^2$


**Q-3 Three equal resistances are connected in series then in parallel. What will be the ratio of their Resistances?**

Ans- $R_{\text{series}} = 3R$ .

$$R_{\text{parallel}} = R/3$$

$$R_{\text{series}} / R_{\text{parallel}} = 3R / (R/3) = 9$$

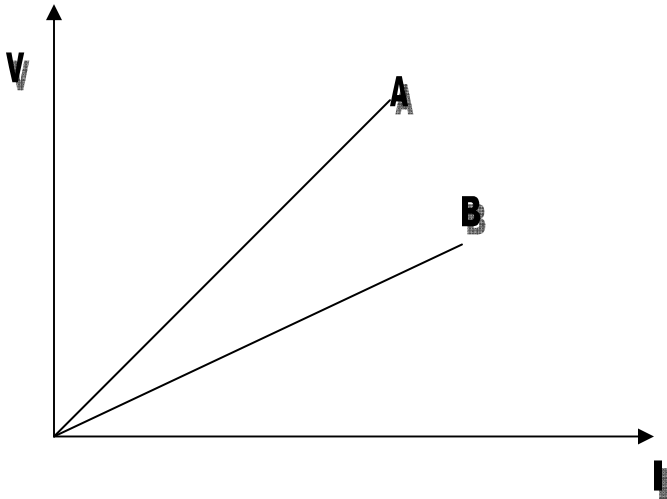**Q-4 Jusitfy for any pair of resistance the equivalent resistance in series is greater equivalent resistance in parallel .**



Ans- Since,  $R = V/I$

$$R_A > R_B$$

A=Series, B=Parallel

**Q-5 How many bulbs of  $8\Omega$  should be joined in parallel to draw a current of 2A from a battery of 4 V?**

Ans- $R = V/I = 4/2 = 2\Omega$ , let 'n' be the no of bulbs.

$$1/R = 1/R_1 + 1/R_2 + \dots + 1/R_n = n/8$$

$$1/2 = n/8, n=4.$$

**Q-6 Two cubes A and B are of the same material. The side of B is thrice as that of A. Find the ratio  $R_A/R_B$ .**

$$\text{Ans-} R_A = \rho L/A \quad R_B = \rho 3L/9A$$

$$R_A : R_B = 3:1$$

**Q-7  $3 \times 10^{11}$  electrons are flowing through the filament of bulb for two minutes. Find the current flowing through the circuit. Charge on one electron =  $1.6 \times 10^{-19}$  C.**

$$\text{Ans-} q = ne = 3 \times 10^{11} \times 1.6 \times 10^{-19} = 4.8 \times 10^{-8} \text{ C}$$

$$I = q/t = 4.8 \times 10^{-8} / (2 \times 60) = 4 \times 10^{-7} \text{ A}$$

**Q-8** A nichrome wire of resistivity  $100 \times 10^{-6} \text{ ohm-m}$  and copper wire of resistivity  $1.62 \times 10^{-8} \text{ ohm-m}$  of same length and same area of cross section are connected in series, current is passed through them, why does the nichrome wire gets heated first?


Ans.  $Q = I^2 R t$

$$Q = I^2 \{ \rho L/A \} t$$

Nichrome wire has higher resistivity than copper wire. Therefore, it is heated first

(3 Marks Questions)

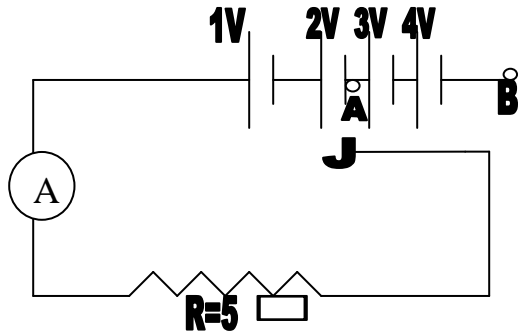**Q1** In the given figure what is ratio of ammeter reading when J is connected to A and then to B



Ans. when J is connected to A

$$I = V/R = 3/5 \text{ A} = 0.6 \text{ A}$$

When J is connected to B

$$V = 1 + 2 + 3 + 4 = 10 \text{ V}$$

$$I = 10/5 = 2 \text{ A}$$