

## Solved Electricity numerical for class 10

1. Question: Two bulbs have ratings 100 W, 220 V and 60 W, 220 V respectively. Which one has a greater resistance?

Answer:  $P=VI=V^2/R$  For the same V, R is inversely proportional to P.

Therefore, the bulb 60 W, 220 V has a greater resistance.

2. Question: A torch bulb has a resistance of  $1\ \Omega$  when cold. It draws a current of 0.2 A from a source of 2 V and glows. Calculate

- (i) the resistance of the bulb when glowing and
- (ii) explain the reason for the difference in resistance.

Answer:

(i) When the bulb glows:

$$V = I R \text{ ---- Ohm's law } R = V/I = 2/0.2 = 10\ \Omega$$

(ii) Resistance of the filament of the bulb increases with increase in temperature. Hence when it glows its resistance is greater than when it is cold.

3. Question: Calculate the resistance of 1 km long copper wire of radius 1 mm. (Resistivity of copper =  $1.72 \times 10^{-8}$ )

Answer:  $L = 1\ \text{km} = 1000\ \text{m}$

$$R = 1\ \text{mm} = 1 \times 10^{-3}$$

$$\rho = 1.72 \times 10^{-8}\ \text{W m}$$

$$\text{Area of cross section} = \pi r^2 = 3.14 \times 10^{-3} \times 10^{-3} = 3.14 \times 10^{-6}$$

$$R = \rho l/A = (1.72 \times 10^{-8} \times 1000) / 3.14 \times 10^{-6} = 5.5\ \Omega$$

4. Question: When a potential difference of 2 V is applied across the ends of a wire of 5 m length, a current of 1 A is found to flow through it. Calculate:

- (i) The resistance per unit length of the wire
- (ii) the resistance of 2 m length of this wire
- (iii) The resistance across the ends of the wire if it is doubled on itself.

Answer: (i)  $V = I R$  ---- Ohm's law  $R=V/I=2/1= 2\ \Omega$

Resistance per unit length:  $2/5= 0.4\ \Omega/\text{m}$

(ii) Resistance of 2 m length of the wire =  $0.4 \times 2=0.8\ \Omega$

(iii) When the wire is doubled on itself:

(a) the area of cross-section is doubled. If A is the original C.S. area, now it is 2 A.

(b) The length becomes half i.e.  $L/2$

Resistance of this wire  $=R' = \rho (l/2)/(2A) = 1/4(\rho(L/A))$

But  $\rho (L/A) = 2 \text{ ohm}$

$R' = 1/4 \times 2 = 0.5 \text{ Ohm}$

5. How much work is done in moving 4 C across two point having pd. 10 v

Solution :  $W = VQ = 10 \times 4 = 40\text{J}$

6. How much energy is given to each coulomb of charge passing through a 9 v battery?

Solution: Potential difference = Work done = Potential difference  $\times$  charge

Where, Charge = 1 C and Potential difference = 6 V

Work done =  $9 \times 1 = 9 \text{ Joule}$ .

7. 100 j of work is done in moving a charge of 5 C from one terminal of battery to another . What is the potential difference of battery?

Solution:  $V = W/Q = 100/5\text{C} = 20 \text{ V}$

8. If  $4 \times 10^{-3} \text{ J}$  of work is done in moving a particles carrying a charge of  $16 \times 10^{-6} \text{ C}$  from infinity to point P .What will be the potential at a point?

Solution: the potential at a point is work done to carry unit from one point to another

$$= (4 \times 10^{-3}) / (16 \times 10^{-6} \text{ C}) = 250 \text{ V}$$

9. Calculate the current and resistance of a 100 W ,200V electric bulb.

Solution: Power,  $P = 100\text{W}$  and Voltage,  $V = 200\text{V}$

Power  $P = VI$

So, Current  $I = P/v = 100/200 = 0.5\text{A}$

Resistance  $R = V/I = 200/0.5 = 400\text{W}$ .

10. Calculate the power rating of the heater coil when used on 220V supply taking 5 Amps.

Solution: Voltage ,  $V = 220\text{V}$  and Current ,  $I = 5\text{A}$ ,

Power,  $P = VI = 220 \times 5 = 1100\text{W} = 1.1 \text{ KW}$ .

11. A lamp can work on a 50 volt mains taking 2 amps. What value of the resistance must be connected in series with it so that it can be operated from 200 volt mains giving the same power.

Solution: Lamp voltage ,  $V = 50\text{V}$  and Current ,  $I = 2 \text{ amps}$ .

Resistance of the lamp =  $V/I = 50 / 2 = 25 \Omega$

Resistance connected in series with lamp =  $r$ .

Supply voltage = 200 volt. and Circuit current  $I = 2 \text{ A}$

Total resistance  $R_t = V/I = 200/2 = 100\Omega$

$$R_t = R + r \quad \Rightarrow \quad 100 = 25 + r \quad \Rightarrow \quad r = 75\Omega$$

12. Calculate the work done in moving a charge of 5 coulombs from a point at a potential of 210 volts to another point at 240 volts

Solution: Potential difference =  $210 - 240 = 30 \text{ V}$

So,  $W = V \times Q = 30\text{V} \times 5\text{C} = 150 \text{ Joules}$

13. How many electrons pass through a lamp in one minute if the current be 200 mA?

Solution:

$$I = 220 \text{ mA} = 0.22 \text{ A}$$

$$I = Q/t$$

$$0.22 = Q/60$$

$$Q = 0.22 \times 60 = 13.2 \text{ C}$$

No of electron carry 1 C charge =  $6 \times 10^{18}$

No of electron carry 13.2 C charge =  $6 \times 10^{18} \times 13.2 \text{ C} = 79.2 \times 10^{18}$

14. Calculate the current supplied by a cell if the amount of charge passing through the cell in 4 seconds is 12 C ?

Solution: We know that  $I = Q/t \Rightarrow I = Q/t = 12/4 = 3\text{A}$

15. A 2 Volt cell is connected to a 1  $\Omega$  resistor. How many electrons come out of the negative terminal of the cell in 2 minutes?

Solution:  $V = IR \Rightarrow I = V/R = 2/1 = 2 \text{ A}$

$$I = Q/t \Rightarrow Q = It = 2 \times 2 \times 20 = 80 \text{ C}$$

No of electron carry 1 C charge =  $6 \times 10^{18}$

No of electron carry 80 C charge =  $6 \times 10^{18} \times 80 \text{ C} = 108 \times 10^{18} = 1.08 \times 10^{20}$

16. (a) How much current will an electric bulb draw from a 220 V source, if the resistance of the bulb filament is 1200  $\Omega$ ?

(b) How much current will an electric heater coil draw from a 220 V source, if the resistance of the heater coil is 100  $\Omega$ ?

Solution (a) We are given  $V = 220 \text{ V}$ ;  $R = 1200 \Omega$ .

we have the current  $I = V/R = 220 \text{ V}/1200 \Omega = 0.18 \text{ A}$ .

(b) We are given,  $V = 220 \text{ V}$ ,  $R = 100 \Omega$ .

we have the current  $I = V/R = 220 \text{ V}/100 \Omega = 2.2 \text{ A}$ .

17. The potential difference between the terminals of an electric heater is 60 V when it draws a current of 4 A from the source. What current will the heater draw if the potential difference is increased to 120 V?

Solution : We are given, potential difference  $V = 60 \text{ V}$ , current  $I = 4 \text{ A}$ .

According to Ohm's law,  $R = V/I = 60/4 = 15\Omega$

When the potential difference is increased to 120 V

the current is given by current =  $V/R = 120V/15 = 8A$

The current through the heater becomes 8 A.

18. A  $4\Omega$  resistance wire is doubled on it. Calculate the new resistance of the wire.

Solution We are given,  $R = 4\Omega$ .

When a wire is doubled on it, its length would become half and area of cross-section would double. T

So, a wire of length  $l$  and area of cross-section  $A$  becomes of length  $l/2$

And area of cross section  $2A$ . we have  $R = \rho(l/A)$

$R_1 = \rho((l/A) / 2A)$  where  $R_1$  is the new resistance.

Therefore,  $R_1/R = \rho((l/A)/2A) / \rho(l/A) = 1/4$

Or,  $R_1 = R/4 = 4\Omega/4 = 1\Omega$

The new resistance of the wire is  $1\Omega$ .

19. A circuit is made of  $0.4\Omega$  wire, a  $150\Omega$  bulb and a  $120\Omega$  rheostat connected in series. Determine the total resistance of the resistance of the circuit.

Solution: Resistance of the wire =  $0.4\Omega$  Resistance of bulb =  $150\Omega$  Resistance of rheostat =  $120\Omega$

In series, Total resistance,  $R = 0.4 + 150 + 120 = 270.4\Omega$

20. A current of 0.2 Ampere flows through a conductor of resistance  $4.5\Omega$ . Calculate the potential difference at the ends of the conductor.

Solution: The potential difference at the ends of the conductor. =  $V = IR = 0.2 \times 4.5 = 0.9 V$

21. A lamp has a resistance of 96 ohms. How much current flows through the lamp when it is connected to 120 volts?

Solution:  $I = V/R = 120/96 = 1.25 A$  [ $V = IR$ ]

The current through the lamp equals 1.25 A.'

22. The manufacturer specifies that a certain lamp will allow 0.8 ampere of current when 120 volts is applied to it.

What is the resistance of the lamp?

Solution:  $V = IR$  So,  $R = V/I = 120/0.8 = 150 W$

23. How much voltage is required to cause 1.6 amperes in a device that has 30 ohms of resistance?

Given:  $V = IR = 1.6 \times 30 = 48 V$

24. How much power is dissipated when 0.2 ampere of current flows through a 100-ohm resistor?

Ans:  $P = V I = IR \times I = I^2 R = 0.2 \times 0.2 \times 100 = 4 W$

25. How much energy is converted by a device that draws 1.5 amperes from a 12-volt battery for 2 hours?

Solution:  $W = Pt$ ,  $P = V I$  So,  $W = VIt = 12 \times 1.5 \times 2 = 36 Wh$